

4.4 Find the worst-case Elmore parasitic delay of an n -input NOR gate.