

Please attach this cover sheet to your completed homework

Homework 1 (Ch. 7)

ECE 311 – Hang Gao

Name: Gianni Avilan

Problem	Course outcome	Grade
1	1.c.	/20
2	1.c.	/20
3	1.c.	/20
4	1.c.	/20
5	1.c.	/10
6	1.c.	/10
TOTAL:		/100

ABET Assessed Outcomes

1.c. Use appropriate models to formulate solutions related to electric circuit problems.

Homework #1

Due date: Sunday, Feb. 1st by 11:59 PM (Electronically – Canvas)

1. (20 points) The voltage and current of an electric load can be expressed by the following equations:

$$v = 340 \sin(628.318t + 0.5236) \text{ V}$$

$$i = 100 \sin(628.318t + 0.87266) \text{ V}$$

Note that the angles are in radians.

Calculate the following:

- The rms voltage
- The frequency of the current
- The phase shift between current and voltage in degrees
- The average voltage
- The load impedance

2. (20 points) An electric load consists of a 4Ω resistance, a 6Ω inductive reactance, and an 8Ω capacitive reactance connected in series. The total impedance of the load is connected across a voltage source of 120V:

- Compute the power factor of the load
- Compute the source current
- Compute the real power of the circuit
- Compute the reactive power of the circuit


3. (20 points) A voltage source $\bar{V} = 120 \angle 30^\circ$ is connected across a circuit consisting of $R = 3.5 \Omega$ in series with $L = 0.0833 \text{ H}$. If the circuit is energized in the united states (the power supply frequency is 60Hz), compute the following:

- The load current
- The load power factor
- The real power consumed by the load
- The reactive power consumed by the load

4. (20 points) A voltage source $\bar{V} = 120 \angle 30^\circ$ is connected to a circuit consisting of $R = 3.5 \Omega$ in series with $L = 0.0833 \text{ H}$. If the circuit is energized in Europe (the power supply frequency is 50Hz), compute the following:

- The load current
- The load power factor
- The real power consumed by the load
- The reactive power consumed by the load

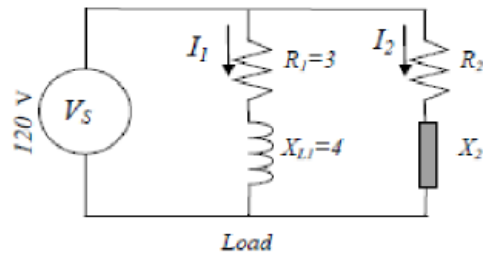5. (10 points) An inductive load consists of $R_1 = 3 \Omega$ in series with $X_{L1} = 4 \Omega$. The load is connected in parallel with another load of unknown impedance ($R_2 + jX_2$). The voltage source of the system is 120V. The total real and reactive powers delivered by the source are 3 kW and 2 kVAR, respectively. Compute the impedance of the unknown load.



- 6.** (10 points) An inductive load consists of $1\ \Omega$ resistance and 1.0mH inductance connected in series. The load is connected across 120V , 60Hz source.
- Compute the power factor of the load.
 - A capacitor is connected in parallel with the entire load so that no reactive power is delivered by the source. Compute the value of the capacitance.