

Please attach this cover sheet to your completed homework

Homework 2 (Ch. 8)

ECE 311 – Hang Gao

Name: Gianni Avilan-Losee

Problem	Course outcome	Grade
8.1	1.c.	/36
8.2	1.c.	/20
8.5	1.c.	/15
8.6	1.c.	/15
8.11	1.c.	/14
TOTAL:		/100

ABET Assessed Outcomes

1.c. Use appropriate models to formulate solutions related to electric circuit problems.

Homework #2

Due date: Sunday, February 8th by 11:59 PM (Electronically – Canvas)

8.1 A Y-connected balanced three-phase source is feeding a balanced three-phase load. The voltage and current of the source coil are

$$v(t) = 340 \sin(377t + 0.5236)V$$

$$i(t) = 100 \sin(377t + 0.87266)A$$

The phase shift angles in the two equations are in radians. Calculate the following:

- The rms phase voltage
- The rms line-to-line voltage
- The rms current in the source
- The rms current in the transmission line
- The frequency of the supply
- The power factor at the source side, state leading or lagging
- The three-phase real power delivered to the load
- The three-phase reactive power delivered to the load
- If the load is connected in delta configuration, calculate the load impedance

8.2 The current and voltage of a wye-connected load are:

$$\bar{V}_{ca} = 480 \angle -60^\circ V$$

$$\bar{I}_b = 20 \angle 120^\circ A$$

- Compute $\bar{V}_{an}$
- Compute $\bar{I}_a$
- Compute the power factor angle
- Compute the real power of the load

8.5 A balanced wye-connected load of $(4+j3)\Omega$ is connected across a three-phase source of 173 V (line-to-line).

- Find the transmission line current
- Find the power factor, the complex power, the real power, and the reactive power of the load.
- With V_{ab} as the reference, sketch the phasor diagram that shows all voltages and currents.

- 8.6** Two three-phase wye-connected loads are in parallel across a three-phase supply. The first load draws a current of 20 A at 0.9 power factor leading, and the second load draws a current of 30 A at 0.8 power factor lagging. Calculate the following:
- The transmission line current
 - The power factor of the load
 - The real power supplied by the source if the line-to-line voltage of the transmission line is 400 V

8.11 A three-phase wye-connected source is energizing a delta-connected load. The phase voltage of the transmission line is $\bar{V}_{bn} = 120 \angle 0^\circ \text{V}$, and the total load impedance is $\bar{Z} = 9 \angle 30^\circ \Omega$. Compute the line current $\bar{I}_a$ and the real power consumed by the delta load.